


The background of the slide features a futuristic theme. On the left, a white and black robotic arm is shown in profile, reaching out towards the center. The background is composed of several elements: a series of white DNA double helix structures on the left, a row of grey server racks on the right, and a central purple band with white circular patterns. The title text is overlaid on this purple band.

ELEC1100: Introduction to Electro-Robot Design

Lecture 6: PWM Motor Control



ELEC1100 ROADMAP

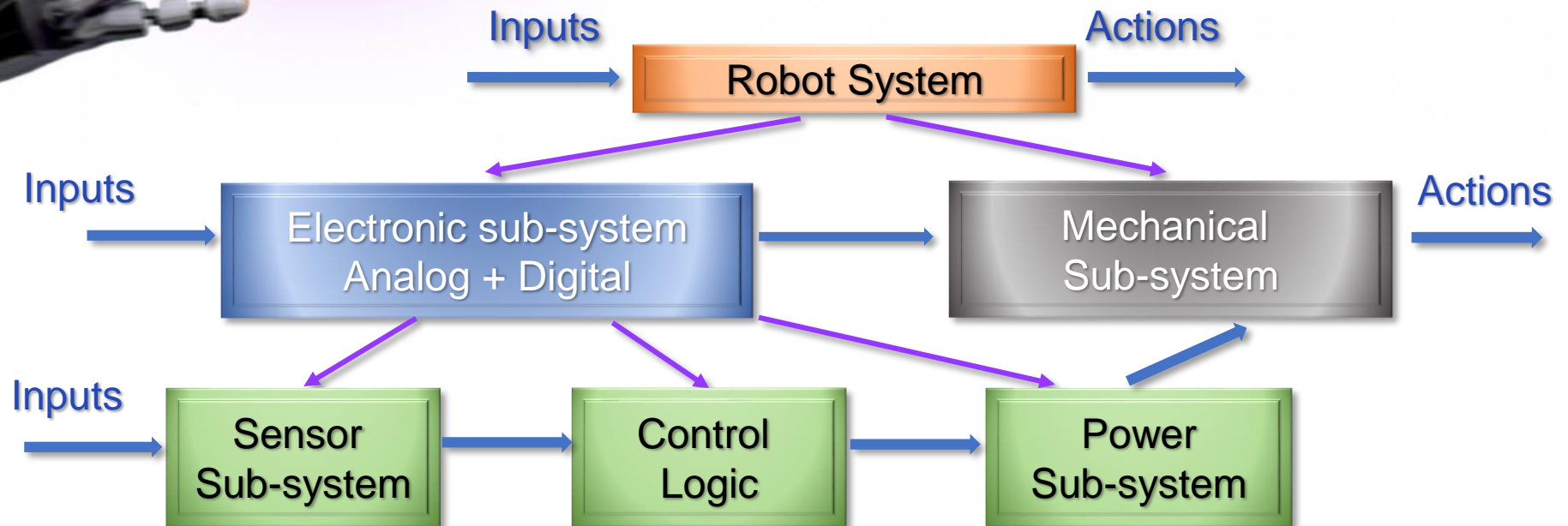

Basic electronics:

- Wk1: Basic Electronics - Charge/Current/Voltage/Resistor
- Wk2: Energy/Power and DC Sources

Motor Power Supply:

- Wk3: Pulse Signal and PWM Control






LAST LECTURE: GENERIC MOTOR SPEED CONTROL

- ❖ Higher voltage leads to larger current, higher power and faster rotation
- ❖ Different voltages can be obtained by using a variable resistor

- ❖ **Disadvantages:**


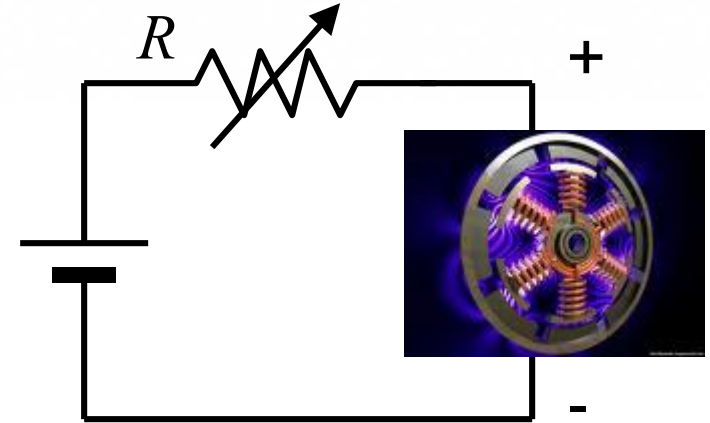
- It is not efficient- energy is wasted as heat in the variable resistor particularly at low speeds.
- It is difficult to control the speed precisely
- Need mechanical motion to tune the resistor and not computer friendly





PULSE WIDTH MODULATION (PWM)

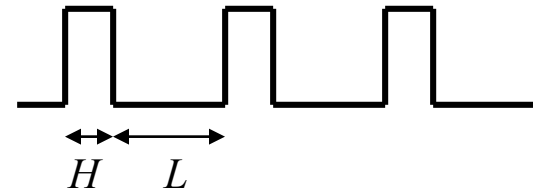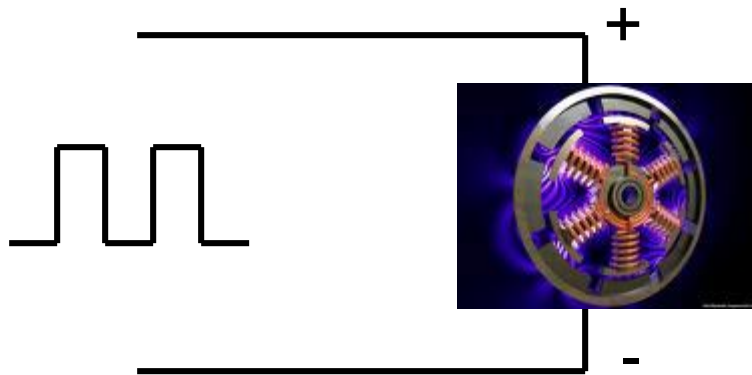- ❖ Turning the motor on/off quickly and repeatedly



$$\text{Period} = H + L$$


$$\text{Duty cycle} = \frac{H}{H + L}$$

- ❖ By adjusting the **duty cycle**, the speed of the motor can be controlled





GENERATING PULSES

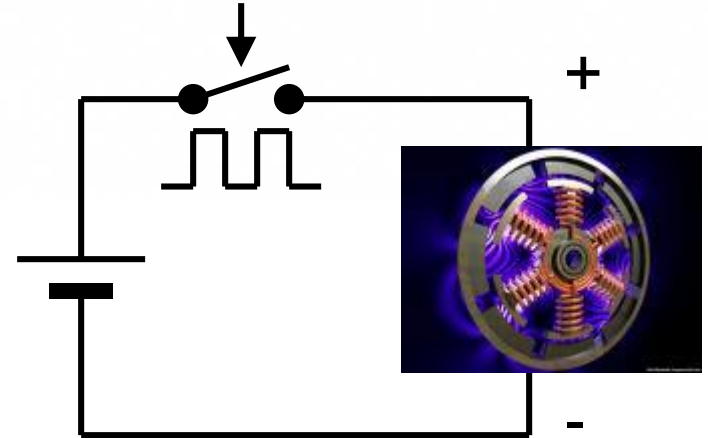- ❖ By mechanically pressing a switch quickly



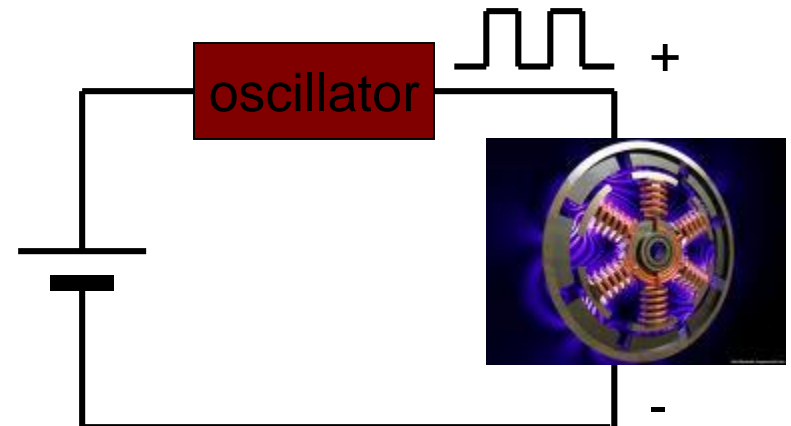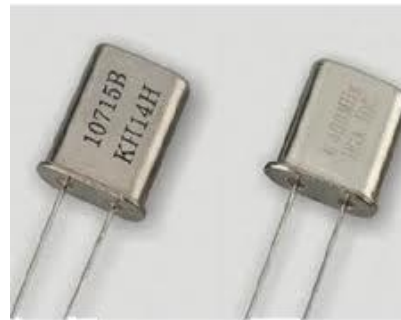
- ❖ By electrical means using an oscillator



555 TIMER

- ❖ Oscillators can also be constructed using a 555 Timer IC (will be used in your project)


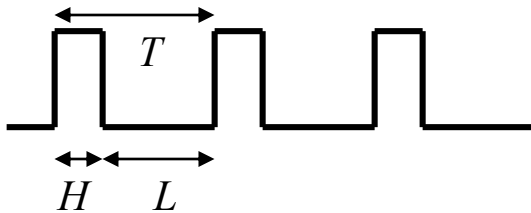
- ❖ The frequency of this clock signal depends on the values of R_A , R_B and C_1 according to the formulas below



$$H = 0.7(R_A + R_B)C_1$$

$$L = 0.7R_B C_1$$

$$T = H + L = 0.7(R_A + 2R_B)C_1$$

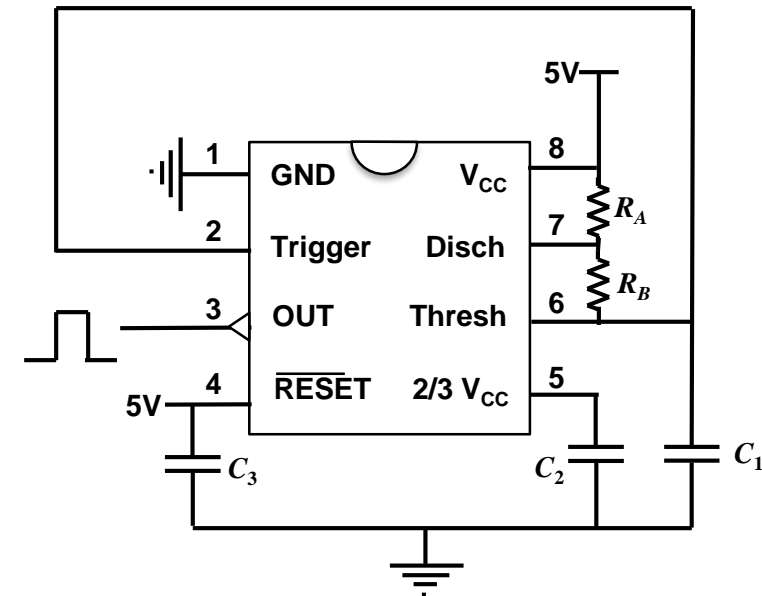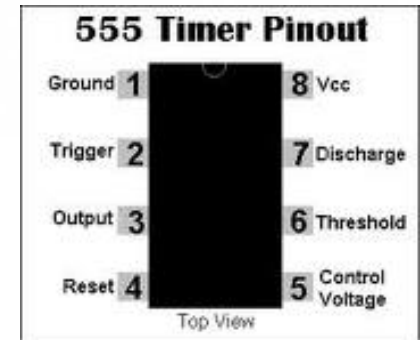




PWM CONTROL WITH NE555

- ❖ Controlling the pulse width with R_A , R_B and C_1 also requires mechanical intervention
- ❖ Analog control also difficult to obtain the required speed precisely



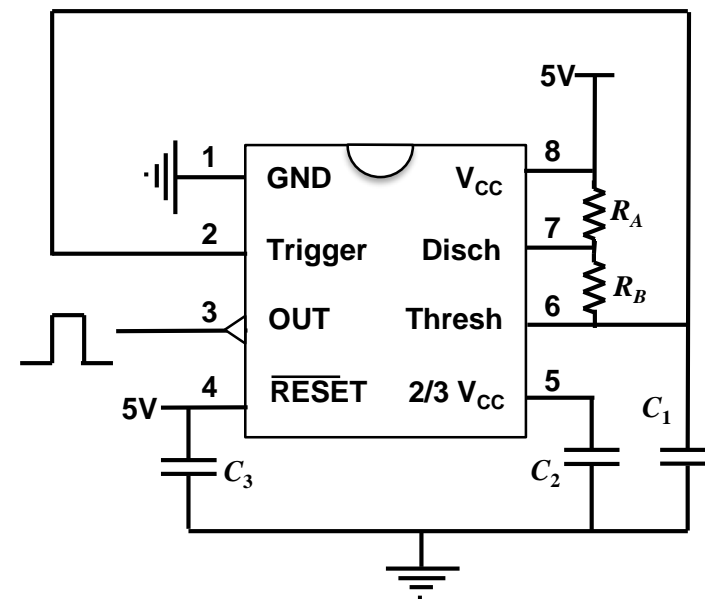
- ❖ We will develop a method to control the pulse width digitally





BINARY NUMBERS

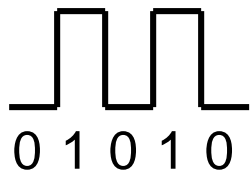- ❖ Decimal number system – base 10, each digital is coming from the set $\{0,1,2,3,4,5,6,7,8,9\}$
- ❖ Binary number system – base 2, each digit is selected from the set $\{0,1\}$
- ❖ Why do we use a binary system?



- It can be represented by two voltage levels


Base 10	Base 2
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
10	1010






PULSE AND BINARY REPRESENTATION

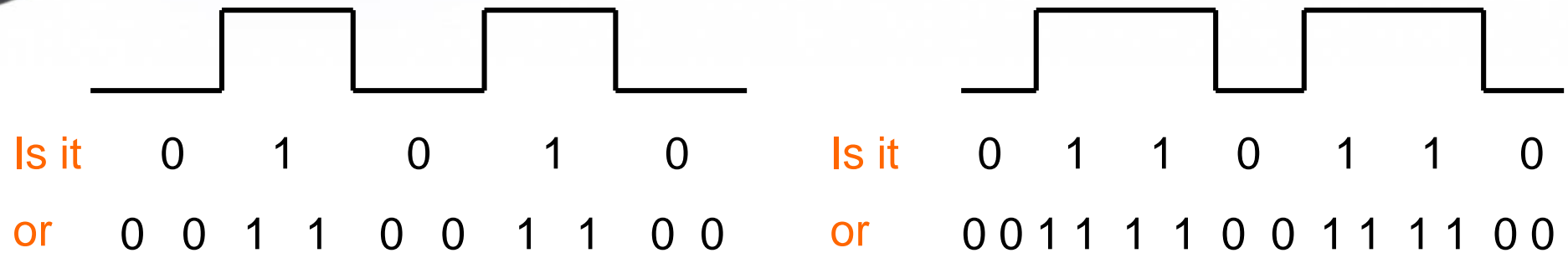❖ You may use pulses to transmit binary numbers ... but



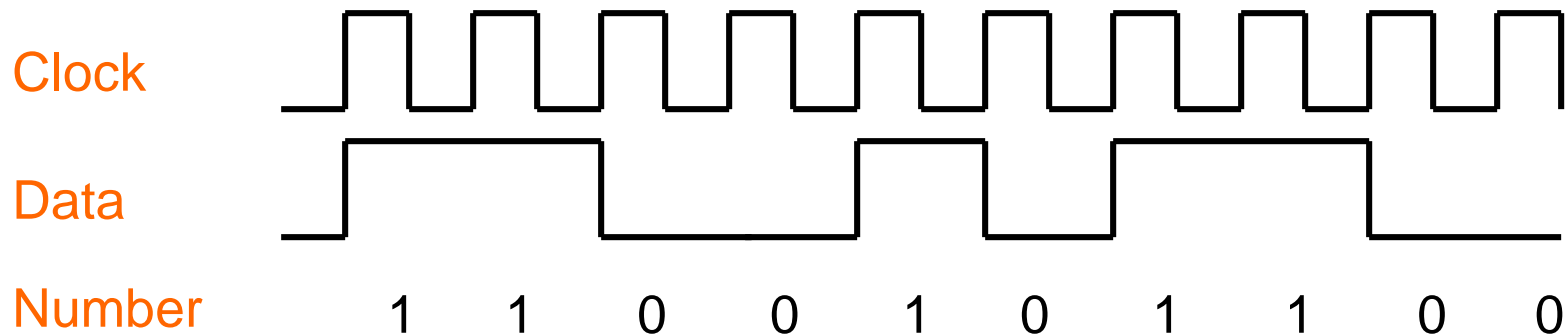❖ A synchronization signal called a “clock” is needed



Q: how can you transmit more bits in the same time slot?





CLOCK


- ❖ A **clock** is a series of pulses transmitted at constant frequency for synchronization
- ❖ Clock speed usually represents the **fastest rate data** that can be handled or transmitted
- ❖ Most electronic systems require clocks
- ❖ Example: Intel Core i7 3.4GHz Quad-Core represents the fastest signal is at **3.4GHz** (or 3,400,000,000 pulses per second)





COUNTER (74HC161)

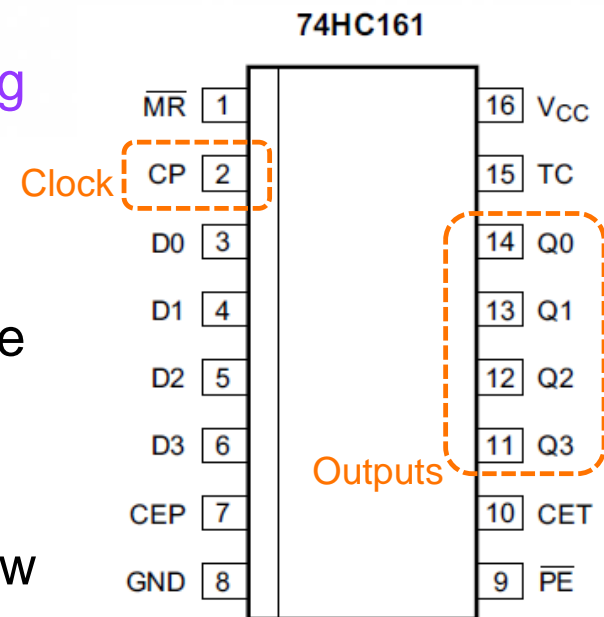
- ❖ A counter is an IC that counts the number of **rising edges** of input clock (for example, **74HC161**)
- ❖ Its output is a binary number $Q_3Q_2Q_1Q_0$
- ❖ Binary number consists of only “0” and “1” and the equivalent decimal number is given below
- ❖ In circuit, “1” represents high and “0” represent low



Dec	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
Bin	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100	1101	1110	1111



OUTPUTS OF 74HC161

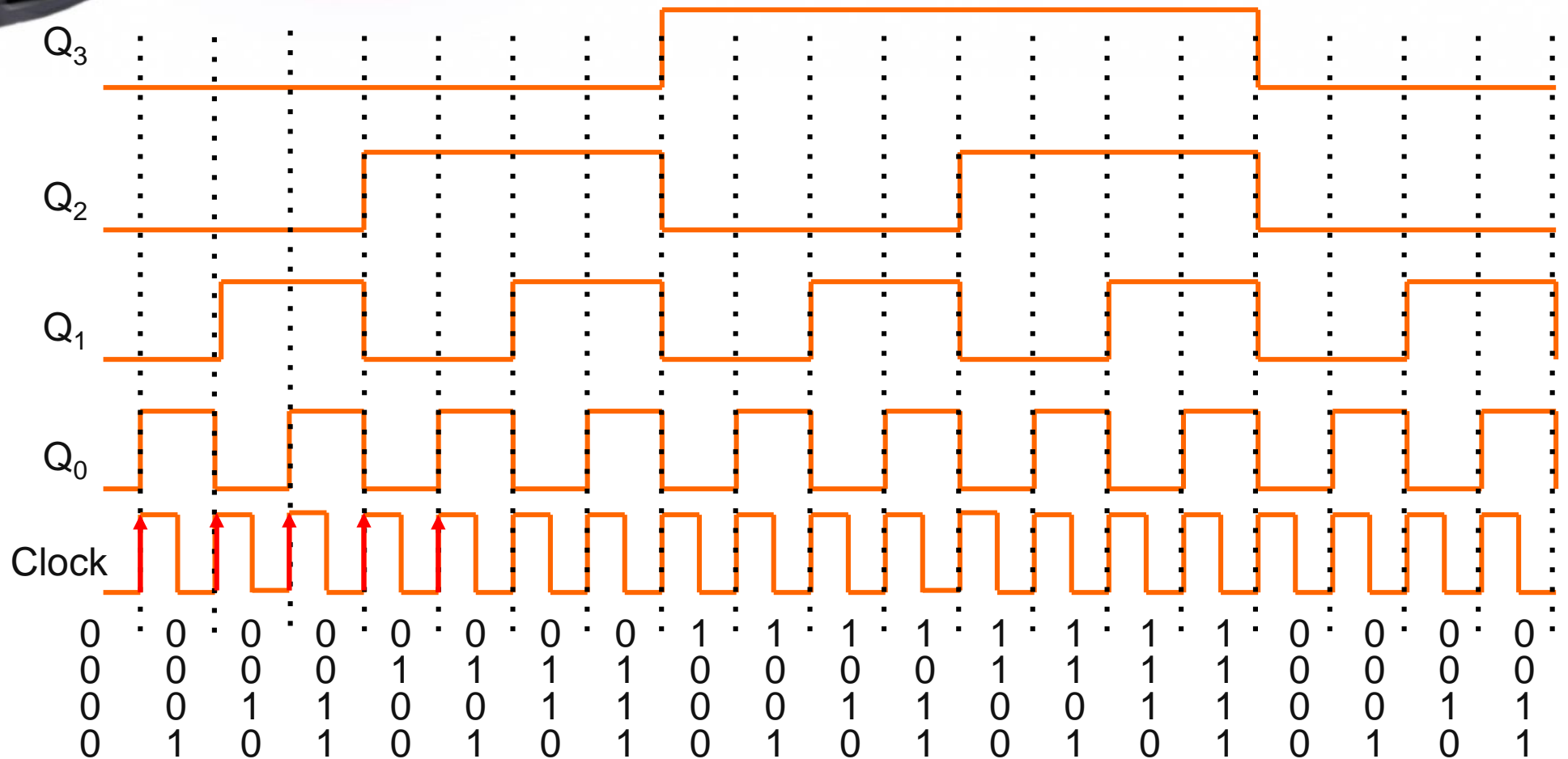



BIT VALUE IN BINARY NUMBER

- ❖ Digit value in decimal number

$$\begin{array}{ccccccccc} \dots & \underline{x} & \underline{x} & \underline{x} & \underline{x} & \underline{x} & & & \\ \dots & 10^4 & 10^3 & 10^2 & 10^1 & 10^0 & & & \end{array}$$

- ❖ Digit value in binary number

$$\begin{array}{ccccccccc} \dots & \underline{x} & \underline{x} & \underline{x} & \underline{x} & \underline{x} & & & \\ \dots & 2^4 & 2^3 & 2^2 & 2^1 & 2^0 & & & \\ \dots & 16 & 8 & 4 & 2 & 1 & & & \end{array}$$

- ❖ For n binary digits, in total it can represent 2^n numbers, the largest number is $2^n - 1$

Q: For 74HC161, the 4-bit binary counter, what is the largest number it can output?

$$\text{Answer: } 2^4 - 1 = 15 \quad (Q_3 Q_2 Q_1 Q_0 = 1111)$$





COMPARATOR (74HC85)


- ❖ A comparator compares 2 binary numbers

$A (=A_3A_2A_1A_0)$ and $B (=B_3B_2B_1B_0)$

- ❖ If $A < B$, the pin $A < B$ will go high and so on

- ❖ Suppose the number A comes from the counter 74HC161 and starting from 0000

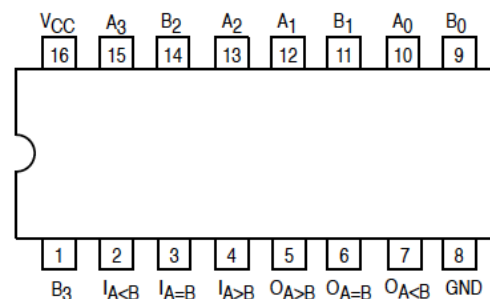- ❖ By inputting a fixed number to B , we can control the duty cycle at output of $A < B$




$O_{A<B}$ output


$B=0$



$B=4$

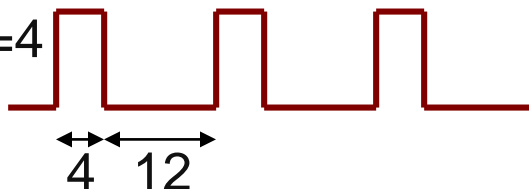


$B=15$

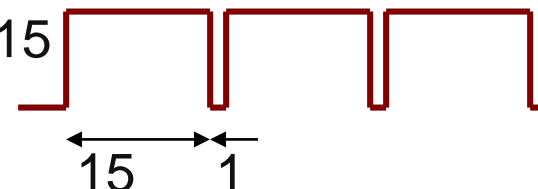



INPUTING TO THE COMPARATOR

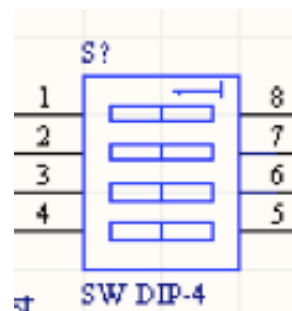- ❖ The input to the **B** value of **74HC85** is done by a **dip switch** to either connect it to ground or power supply



- ❖ Now you have a **vague idea** of the method to control pulse width (which you will do in **Lab#03**)
- ❖ It is time to put everything together



Lab#03


The circuit diagram illustrates a 4-bit comparator system. It consists of three main integrated circuits: a 74HC14 (Schmitt trigger inverter), a 74HC161 (4-bit counter), and a 74HC85 (4-bit comparator). The 74HC14 is configured as a buffer/inverter. The 74HC161 is a 4-bit counter with outputs Q0, Q1, Q2, and Q3. The 74HC85 is a 4-bit comparator with inputs P0, P1, P2, and P3, and outputs O(P<Q), O(P=Q), and O(P>Q). The circuit is powered by a +5V supply and ground. A 0.1uF capacitor is connected to the VCC pin of the 74HC14. A 5K resistor (VR1) is connected to the output of the 74HC14. A switch (SW1) is connected to the output of the 74HC161. The comparator outputs are labeled O(P<Q), O(P=Q), and O(P>Q). The circuit is labeled "Pulse Width Modulation" and "Pulse Width Modulation outputs".





THE TTL IC (7400 SERIES)

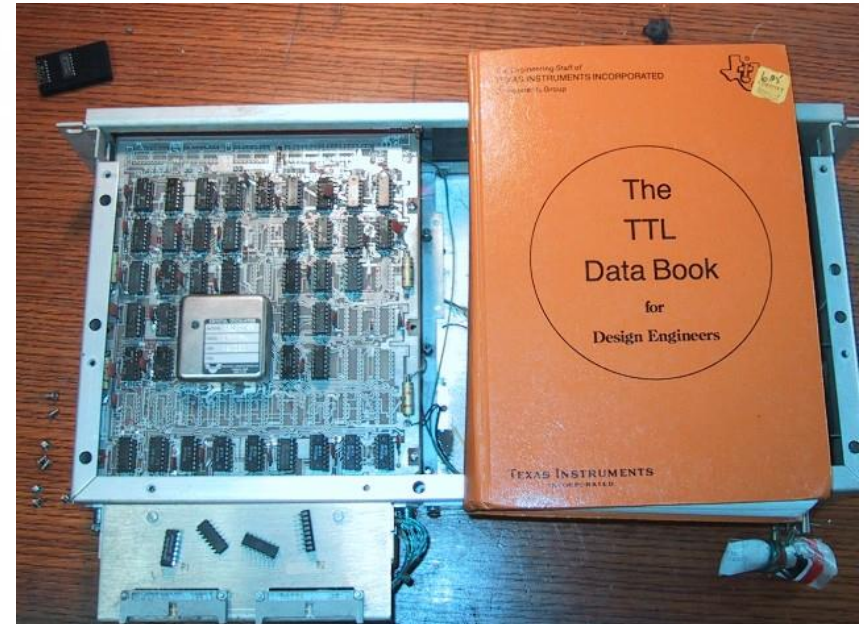
- ❖ The most widely used series to provide various functions to handle digital pulses
- ❖ Mainly developed by Texas Instruments (TI) with many compatible parts from AMD, Fairchild, Intel, Intersil, etc.
- ❖ Number with *74xx*, *74Lxx*, *74Hxx*, *74Sxx*, *74LSxx*
- ❖ Functionality can be easily found from the internet





TWO MOTORS FOR YOUR CAR

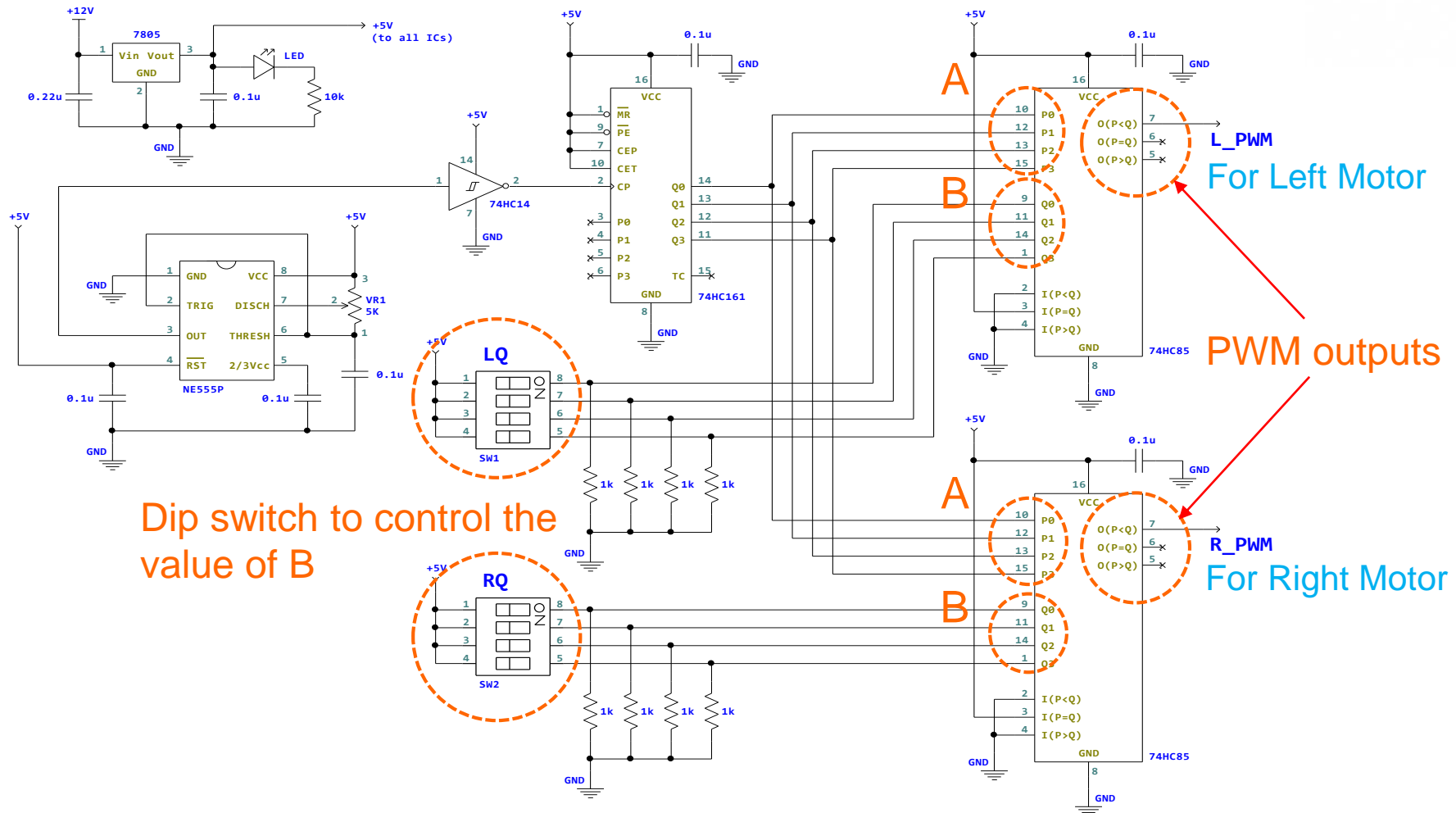❖ You are going to construct the following circuit in **Lab#04**





LECTURE SUMMARY

- ❖ Even though the circuit diagram is a bit complicated, the final circuit is not that difficult to construct.
- ❖ Be patient and work carefully, you will be able to get the circuit working.
- ❖ Arrange your breadboard nicely for the future labs.





NEXT LECTURE

❖ Transistors and switches



QUESTIONS?

